

Lab Report 5: Op-Amp Applications

Submitted By:

Krishna Patil (EE24BTECH11036)

Deepak Kumar Ahirwar (EE24BTECH11014)

**Department of Electrical Engineering
IIT Hyderabad**

March 1, 2025

Objective

To study the applications of operational amplifiers (Op-Amps) by implementing:

- Custom weighted summing and difference amplifier
- Op-Amp integrator
- Precision rectifier (Super Diode)

Apparatus

- Operational Amplifiers (LM358, LM741, TL081)
- Resistors (selected for proper weighting and circuit operation)
- Capacitors (for integration circuit)
- Diodes (e.g., 1N4148 for rectification)
- DC power supply
- Function generator
- Oscilloscope

Theory

1. Custom Weighted Summing and Difference Amplifier

A summing amplifier combines multiple inputs with specified gains. Using an inverting summing amplifier configuration:

$$V_{out} = - \left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right) \quad (1)$$

For specific resistor values, the desired expressions can be achieved:

$$V_{out} = 2V_1 + V_2 - V_3 \quad (2)$$

$$V_{out} = 2V_1 - V_3 \quad (3)$$

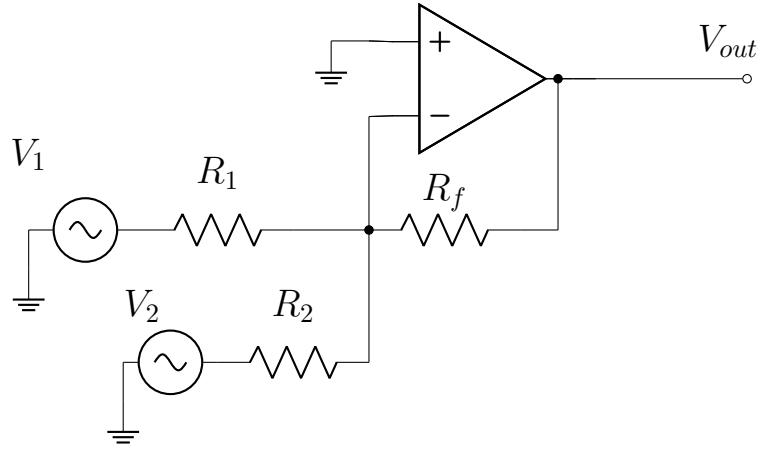


Figure 1: Summing and Difference Amplifier Circuit

2. Op-Amp Integrator

An Op-Amp integrator mathematically integrates the input signal:

$$V_{out} = -\frac{1}{RC} \int V_{in} dt \quad (4)$$

It converts a square wave input into a triangular wave output and is useful in signal processing applications.

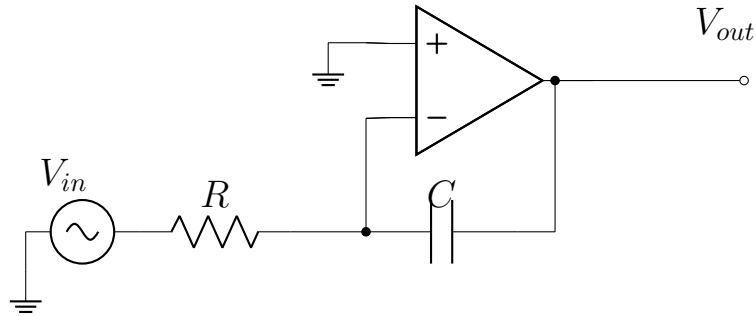


Figure 2: Op-Amp Integrator Circuit

3. Precision Rectifier (Super Diode)

A precision rectifier eliminates the 0.7V drop of standard diodes by using an Op-Amp:

$$V_{out} = \begin{cases} 0, & V_{in} < 0 \\ V_{in}, & V_{in} > 0 \end{cases} \quad (5)$$

For a full-wave rectifier, an additional summing stage is used to combine positive and inverted negative portions.

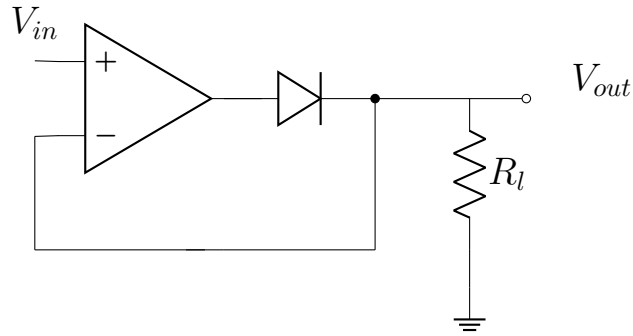


Figure 3: Precision Rectifier Circuit

Procedure

1. Assemble each circuit as per the given schematics.
2. Apply appropriate input signals using a function generator.
3. Measure output using an oscilloscope.
4. Compare theoretical and experimental results.
5. Record observations and plot graphs.

Observations

Summing and Difference Amplifier

$$R_1 = R_2 = 2k\Omega, R_3 = 1k\Omega$$

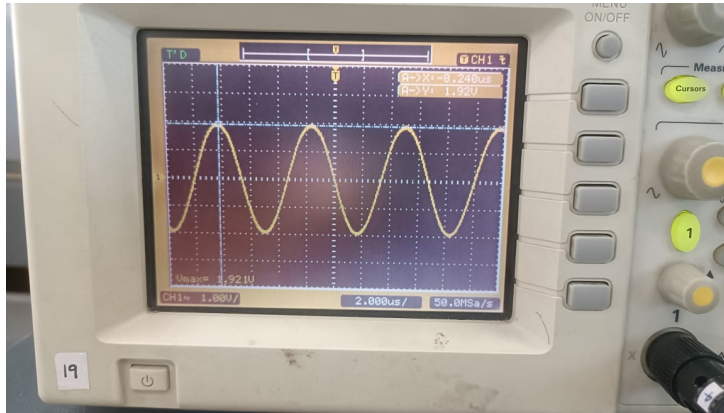


Figure 4: $V_1 = V_2 = \sin(2\pi ft)$ $f = 150kHz$



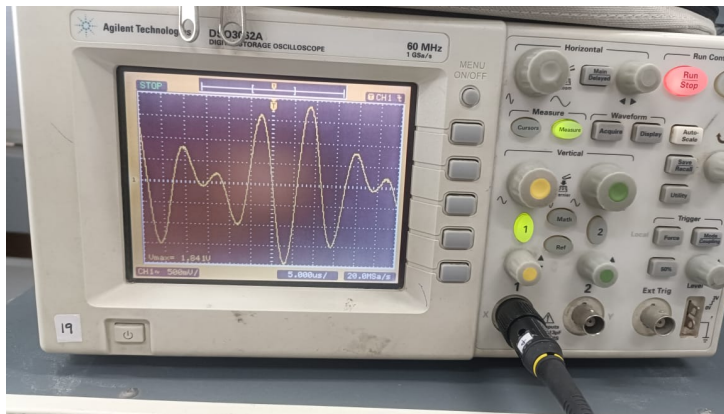


Figure 5: $V_1 = \sin(2\pi f_1 t)$, $V_2 = \sin(2\pi f_2 t)$, $f_1 = 75kHz$, $f_2 = 100kHz$

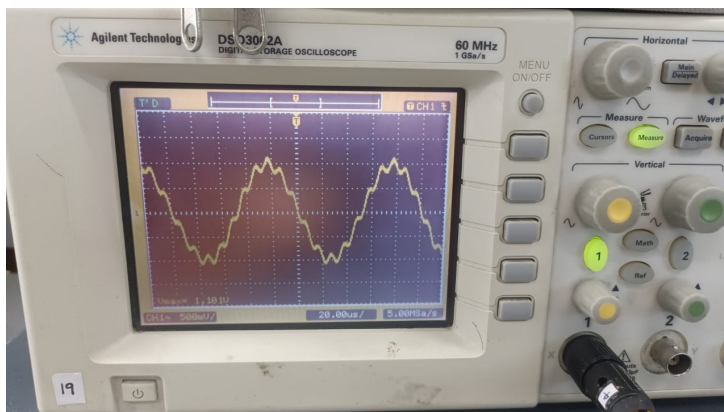

Op-Amp Integrator

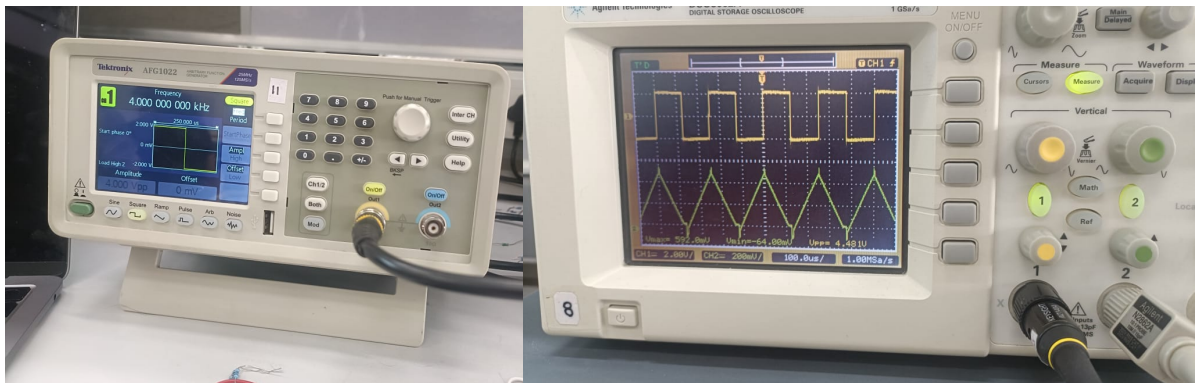

Precision Rectifier

